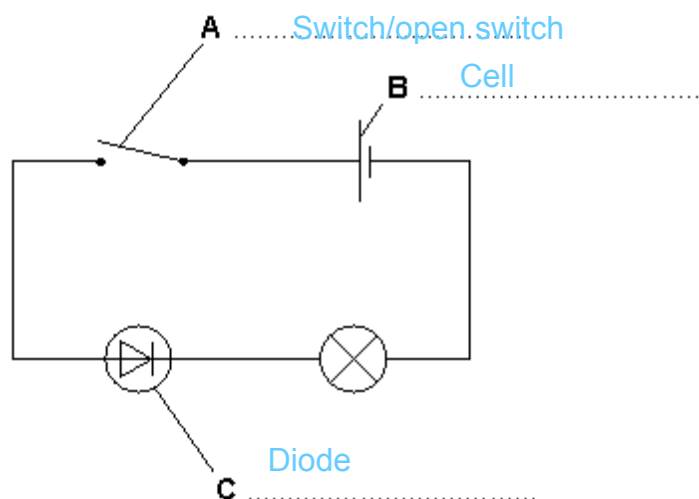



- 1 Label the components, A, B, and C, in the circuit diagram.



(3 marks)

Total 3 marks

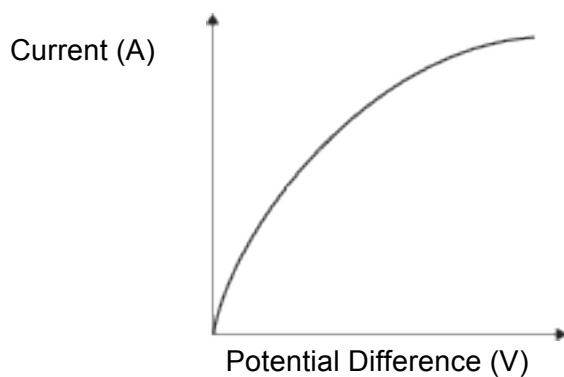- 2 The diagram shows the circuit used to obtain the data needed to plot the current–potential difference graph for a filament bulb.



- 2 (a) (i) What is the meaning of the following terms:

Potential Difference

Work done (energy transferred) per coulomb of charge [1 mark]

Current

The flow of charge or the flow of electrons. [1 mark]

(2 marks)

- 2 (a) (ii) The resistance of the metal filament inside the bulb increases as the potential difference across the bulb increases.

Explain why.

Metals contain free electrons (and ions) [1 mark]

As temperature of filament increases ions or atoms vibrate faster / with a bigger amplitude or vibrate more [1 mark]

Electrons collide more (frequently) with the ions or (drift) velocity of electrons decreases [1 mark]

(3 marks)


- 2 (a) (iii) The bulb is operating at a potential difference of 12V. Calculate the power of the bulb when the current through it is 2A. Use the correct equation from the Physics Equations Sheet.

The correct equation is $P = V \times I$

12 x 2 [1 mark]

There are usually no marks for
writing the correct equation.Power =24..... W
(3 marks)**Total 8 marks**

- 3 The diagram shows the circuit used to investigate the resistance of a fixed resistor. The ammeter and voltmeter are missing.

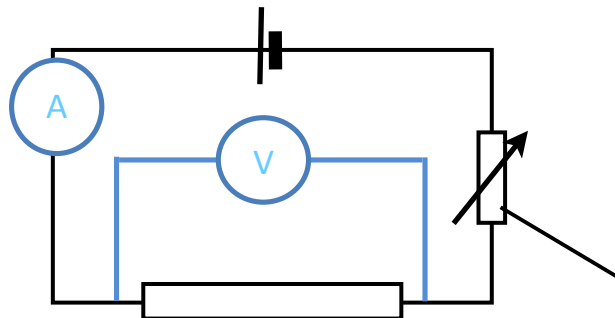

Component X

- 3 (a) (i) Draw the symbols for the ammeter and voltmeter on the diagram in the correct places.

The ammeter can go anywhere along the main circuit.

(2 marks)

- 3 (a) (ii) What is the purpose of component X in this circuit?

To change/vary the current.

(1 mark)

- 3 (a) (iii) The resistance of the fixed resistor can be calculated using readings from the voltmeter and the ammeter.

Calculate the resistance of the resistor when the reading on the voltmeter is 6 volts and the current is 0.2 A. **Give the correct unit.**

Use the correct equation from the equation sheet to help you.

Show you working.

$V = IR$ is the correct equation but it needs to be rearranged to $R = V/I$

$6 / 0.2 =$ [1 mark]

30 [1 mark]

Ohms (or Ω) [1 mark]


Resistance =30 Ohms (or Ω)

(3 marks)

Total 6 marks

Electrical Circuits (questions for 5 videos) 4

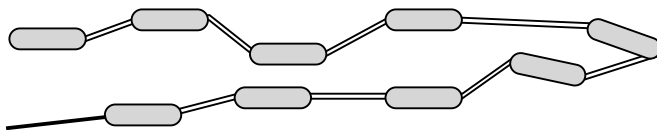- 4 A set of decorative lights is made from nine identical lamps connected in series.



Each lamp is designed to take a current of 0.5 A. The set plugs directly into the 230 V mains electricity supply.

- 4 (a) (i) Calculate the resistance of **one** of the lamps.

Use the correct equation, from the equations sheet.

Show clearly how you work out your final answer and give the unit.


$V = IR$ is the correct equation but it needs to be rearranged to $R = V/I$

$$230 / 0.5$$

$$460$$

Ohms (or Ω) [1 mark]

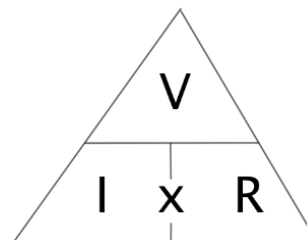The formula triangle would be useful here.



$$\text{Resistance} = \dots\dots\dots 460 \text{ ohms} \dots\dots\dots$$

(3 marks)

- 4 (a) (ii) What is the total resistance of the set of lights?

$$4140$$


or

$$9 \times \text{the answer from 4 (a) (i)}$$

(1 mark)

(Total 7 marks)

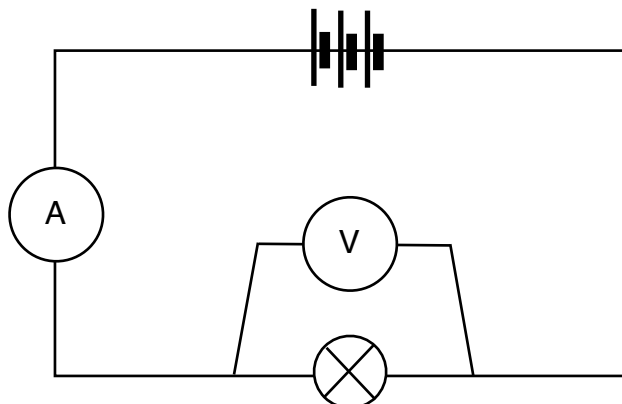- 5 The diagram shows a circuit that lights a lamp. The ammeter measures the current flowing in the circuit.



- 5 (a) (i) What could be done to decrease the brightness of the **given lamp** in the circuit?

Decrease the number of cells
or
Add a resistor/another component

(1 mark)

- 5 (a) (ii) In the circuit above, the lamp transfers 36 Joules of energy when 4 coulombs of charge pass through it.

Calculate the reading on the voltmeter.

Use the correct equation from the equation sheet.

Show your working clearly.

The correct equation is $V = W / Q$ (no marks for writing this out)

$36 / 4$ [1 mark]

9 V [1 mark]

(2 marks)

5 (a) (iii) Calculate the current in the circuit if the charge of 4 coulombs passes the ammeter in 4 seconds.

Calculate the reading on the ammeter.

Use the correct equation from the equation sheet.

Show your working clearly.

The correct equation is $I = Q / t$ (no marks for writing the equation)

4 / 4 [1 mark]

1 A or amp [1 mark]

(2 marks)

(Total 5 marks)

- End of questions -